

Contents

Volume - I

Chapter 1

Electrical Circuit Concepts	1
1.1 Introduction	1
1.2 Network Model	1
1.3 Network Variables	2
1.4 Network Elements	5
1.4.1 Active Elements : Voltage and Current Sources	6
1.4.2 Passive Elements	8
1.5 R-L-C Elements	9
1.5.1 The Resistor	9
1.5.2 The Inductor	12
1.5.3 The Capacitor	16
1.6 Electrical Network	22
1.7 Kirchhoff's Laws	23
1.7.1 Kirchhoff's Current Law	23
1.7.2 Kirchhoff's Voltage Law	24
1.8 Resistive Networks	25
1.8.1 Resistors in series	25
1.8.2 Resistors in Parallel	28
1.8.3 The Voltage Divider	30
1.8.4 The Current Divider	31
1.8.5 Ladder Network	32

1.8.6	Source transformations	34
1.8.7	Voltage source with no series resistance	35
1.8.8	Current source with no parallel resistor	36
1.8.9	Voltage sources with parallel resistors or current sources	37
1.8.10	Current sources in series with resistors or voltage sources	37
1.8.11	Star – Delta or Y – D Transformation	42
1.9	Analysis of Networks	48
1.9.1	Node voltage method	48
1.9.2	Mesh current method	54
1.9.3	Dummy mesh current method	58
	<i>Problems</i>	61

Chapter 2

Single Phase Circuits

2.1	Introduction	70
2.2	Characteristics of Periodic Functions	70
2.3	Average Value, R.M.S Value, form Factor	72
2.3.1	Average value	72
2.3.2	Effective value or RMS value	73
2.3.3	Form Factor	76
2.4	Representation of a sine function	76
2.4.1	Trigonometric representation	77
2.4.2	Phasor representation	77
2.4.3	Complex algebra representation	78
2.5	Steady State Response of R, L and C Elements to Sinusoidal Excitations	81
2.5.1	Response of Pure Resistance	81
2.5.2	Response of pure inductance	83
2.5.3	Response of a pure capacitor	86
2.5.4	Series R – L circuit :	89
2.5.5	Series RC circuit	93
2.5.6	Series RLC circuit	95
2.5.7	Parallel RL circuit	97
2.5.8	Parallel R C circuit	98

2.6	Series Resonance	106
2.6.1	Characteristics of a series resonant circuit	106
2.6.2	Q – factor	110
2.6.3	Selectivity and Bandwidth	112
2.6.4	Voltage across the capacitor	114
2.6.5	Voltage across the inductor	115
2.6.6	Resonance by varying capacitance	116
2.7	Parallel Resonance	118
2.7.1	Maximum impedance by adjusting frequency	120
2.7.2	Selectivity and bandwidth	121
2.8	Locus Diagrams	123
2.8.1	Impedance locus of series connected elements	124
2.8.2	Admittance locus of series connected elements	124
2.8.3	Admittance locus of parallel connected elements	126
2.8.4	Impedance locii of parallel connected elements	127
2.8.5	Current locus of a parallel circuit with one variable branch	127
2.8.6	Inversion of circle	129
	<i>Problems</i>	131

Chapter 3

Magnetic Circuits

3.1	Introduction	138
3.2	Magnetic Fields	138
3.3	Some Definitions	139
3.4	Properties of Magnetic Materials	140
3.4.1	B-H curves	140
3.4.2	Classes of magnetic materials	141
3.5	Faraday's law of electromagnetic induction	141
3.6	Self Inductance	142
3.7	Mutual Inductance	142
3.7.1	Dot convention	143
3.7.2	Energy Consideration in the Magnetically Coupled Coils	145
3.8	Analysis of Simple Magnetic Circuits	148
3.8.1	Leakage flux and leakage coefficient	149
3.8.2	Composite magnetic circuits	150
	<i>Problems</i>	153

Chapter 4

Network Topology and Analysis and Networks

4.1	Introduction	157
4.2	The Concept of a Network Graph	157
4.2.1	Chords or Links	162
4.3	Network Matrices	162
4.3.1	Incidence Matrix (A)	162
4.3.2	Circuit Matrix or Tie set Matrix B	165
4.3.3	Cutset matrix Q	167
4.4	Network Analysis	169
4.5	Duality and Dual Networks	174
4.5.1	Formulation of network equations	174
4.5.2	Duality	176
	<i>Problems</i>	181

Chapter 5

Network Theorems

(With Both DC and AC Excitations)

5.1	Introduction	185
5.2	General Network Equations	185
5.3	Superposition Theorem	187
5.4	Thevenin's Theorem	193
5.5	Norton's Theorem	195
5.6	Millman's Theorem	202
5.7	Reciprocity Theorem	205
5.8	Compensation Theorem	207
5.9	Tellegen's Theorem	212

5.10	Maximum Power Transfer Theorem	216
5.10.1	When source has internal resistance and the load is purely resistive	216
5.10.2	When source has an impedance and the load has variable impedance	217
5.10.3	When source has impedance and the load is purely resistive ...	218
	<i>Problems</i>	224

Volume - II

Chapter 6

Three Phase Circuits

6.1	Introduction	231
6.2	Advantages of Three Phase Over Single Phase	231
6.3	Generation of Three Phase Voltages	232
6.4	Interconnection of Three Phase Windings	233
6.4.1	The Star Connection	234
6.4.2	The Delta Connection	236
6.5	Analysis of 3 Phase Networks	238
6.5.1	Balanced star connected load supplied from Balanced 3 phase 4 wire supply	238
6.5.2	Balanced star connected load supplied from a balanced 3 phase 3 wire supply	240
6.5.3	Power in a star connected system	243
6.5.4	Balanced Δ – connected load connected to a 3-phase balanced supply	244
6.5.5	Power in a Δ – connected balanced system	246
6.6	Unbalanced Three Phase Network	249
6.6.1	Unbalanced star connected load supplied from a 3-phase balanced 4-wire supply	249
6.6.2	Unbalanced Δ – Connected Load	250
6.6.3	Unbalanced Star Connected Load Supplied From a 3 phase balanced 3 wire supply	252
6.7	Measurement of Three Phase Power	257
6.7.1	Two Wattmeter Method	258
6.7.2	Wattmeter Readings and Power Factor in a Balanced Load	259
	<i>Problems</i>	267

Chapter 7**Differential Equations and
Initial Conditions in RLC Networks**

7.1	Introduction	270
7.2	Formulation of Network Equations	270
7.3	Initial Conditions in Networks	274
7.3.1	Behaviour of R, L and C at $t = 0$	275
7.3.2	Behaviour of R, L and C at $t = \infty$	277
7.3.3	Special cases	287
	<i>Problems</i>	295

Chapter 8**Response of RLC Networks**

8.0	Response of R L C Networks	301
8.1	Types of Energy Sources	301
8.2	Response of RL Networks	304
8.2.1	Internal Energy Excitation	304
8.2.2	Unit Impulse Excitation	306
8.2.3	Unit Step Excitation	307
8.2.4	Sinusoidal Excitation	310
8.3	Response of RC Networks	312
8.3.1	Internal Energy Excitation	312
8.3.2	Impulse Excitation	313
8.3.3	Unit Step Excitation	314
8.3.4	Sinusoidal Excitation	315
8.4	Response of RLC Networks	322
8.4.1	Internal Energy Excitation	323
8.4.2	Impulse Excitation	330
8.4.3	Unit step Excitation	331
8.4.4	Sinusoidal Excitation	333

8.5	Laplace Transform Method of Analysis of Networks	338
8.5.1	Introduction	338
8.5.2	The Laplace Transformation	339
8.5.3	Application to Solution of Differential Equations	341
8.5.5	Application to Networks	344
8.6	Transform Networks	346
8.6.1	Resistance	346
8.6.2	Inductance	347
8.6.3	Capacitance	348
8.6.4	Solution of Transform Networks	349
	<i>Problems</i>	355

Chapter 9

Two Port Networks

9.1	Introduction	368
9.2	Two Port Networks	369
9.3	Open Circuit Impedance Parameters	370
9.4	Short Circuit Admittance Parameters	371
9.5	Transmission Parameters	376
9.6	Hybrid Parameters or h – parameters	377
9.7	Relationships between Different Sets of Parameters	380
9.7.1	Relation between y and z – Parameters	380
9.7.2	Transmission Parameters to z – Parameters	381
9.7.3	h – parameters to z – parameters	381
9.7.4	Inverse Hybrid Parameters to z – parameters	382
9.8	Reciprocity and symmetry	383
	<i>Problems</i>	391

Chapter 10

Fourier Series and Fourier Transforms

10.1	Introduction	397
10.2	Fourier Series	397

10.3	Convergence of Fourier Series	402
10.4	Symmetry Conditions in Fourier Series	403
10.4.1	Even Function Symmetry	404
10.4.2	Odd Function symmetry	407
10.4.3	Halfwave or Rotation symmetry	408
10.4.4	Quarterwave symmetry	411
10.4.5	Concealed Symmetry	413
10.5	Complex Fourier Series	415
10.5.1	Some Comments About Complex Fourier Series	418
10.6	Fourier Transforms	424
10.6.1	Existence of the Fourier transform	426
10.7	Fourier Transform Properties	434
10.8	Application to Networks	448
10.8.1	Periodic input functions	448
10.8.2	Pulse input functions	450
	<i>Problems</i>	451
	Answers to Problems	459
	Multiple Choice Questions (MCQs) for Competitive Examinations	477
	Answers to MCQs for Competitive Examinations	595