

Contents

Preface..... (vii)

Acknowledgement..... (ix)

UNIT - I

CHAPTER 1

BASICS OF ELECTRICAL ENGINEERING

1.1	INTRODUCTION	1
1.2	CURRENT FLOW	1
1.2.1	POTENTIAL AND POTENTIAL DIFFERENCE	1
1.2.2	Electric Current	3
1.2.3	Resistance or Resistance Parameter	4
1.2.4	Effect of Temperature on Resistance	8
1.2.5	Electrical Conductance	9
1.3	SOURCES OF ELECTRICAL ENERGY	10
1.3.1	The Voltage Source	10
1.3.2	Current Source	11
1.3.3	D.C. & A.C. Sources	12
1.4	OHM'S LAW	14
1.4.1	Linear & Non-Linear Resistances	15
1.5	ELECTRICAL POWER	17
1.6	ENERGY CALCULATIONS	18

1.7. ELECTRICAL ENERGY	19
1.8 KIRCHOFF'S LAWS	20
1.8.1 Kirchoff's Voltage Law (KVL).....	20
1.8.2 Kirchoff's Current Law (KCL or KIL)	21
1.9 RESISTANCES IN SERIES	26
1.10 RESISTANCES IN PARALLEL	30
1.10.1 Division of Currents in Parallel Circuits	32
1.11 SERIES-PARALLEL RESISTANCES.....	36
1.12 RESISTANCES IN STAR OR DELTA CONNECTIONS	41
1.12.1 The Equivalent Star Resistances For Given Delta Connected Resistances ..	42
1.12.2 The Equivalent Delta Resistances For Given Star Connected Resistances ..	43
1.13 FEATURES OF A RESISTANCE	49
1.14 USES OF RESISTANCE	50
1.15 DIFFERENCES BETWEEN ELECTRICAL & ELECTRONIC CIRCUITS.....	51
1.16 NETWORK THEOREMS.....	52
1.16.1 Introduction to Network Theorems	52
1.17 NETWORK CLASSIFICATION.....	53
1.17.1 Linear Networks	53
1.17.2 Passive Networks	53
1.17.3 Lamped Networks	54
1.17.4 Bilateral Networks	55
1.17.5 Time Invariant Networks	55
1.17.6 Reciprocity	55
1.18 SUPERPOSITION THEOREM	56
1.19 THEVENIN'S THEOREM	58
1.20. NORTON'S THEOREM	63
1.21 MAXIMUM POWER TRANSFER THEOREM.....	65
COMPREHENSION - 1	69
EXERCISE - 1	72

CHAPTER 2

D.C. CIRCUIT ANALYSIS USING MESH AND NODAL ANALYSIS

2.1	INTRODUCTION	81
2.1.1.	Controlled or dependent voltage and current sources :	82
2.1.2	Controlled Source or Dependent Source	82
2.1.3.	Controlled Voltage Source	82
2.1.4	Controlled Current Source	83
2.1.5	Combination of Energy Sources	84
2.1.6	Voltage Sources in Series	84
2.1.7.	Current Sources in Parallel	84
2.1.8	Voltage Sources in Parallel and Current Sources in Series & Parallel ...	85
2.1.9	Source Transformations	86
2.1.10	Source Shifting	87
2.2	LOOP OR MESH ANALYSIS AND NODAL ANALYSIS	90
2.3	LOOP ANALYSIS FOR D.C. CIRCUITS	90
2.3.1	Redundant Elements	91
2.3.2	Identification of independant loops	91
2.3.3	Loop Analysis Using Independent Voltage Sources	92
2.3.4	Loop Analysis Using Independent Current Sources (Super Mesh)	95
2.3.5	Loop Analysis using Independent Voltage and Current Sources	96
2.4.	NODAL ANALYSIS	99
2.4.1	Identification of Independant Nodes	100
2.5	NODAL ANALYSIS FOR D.C. CIRCUITS	101
2.5.1	Nodal Analysis using Independent Current Sources	101
2.5.2	Nodal analysis using Independent Voltage Sources (Super Nodes)	103
2.5.3	Nodal Analysis using Independent Voltage and Current Sources	105
2.6	NODAL ANALYSIS WITH DEPENDENT SOURCES	112
	COMPREHENSION-2	113
	EXERCISE-2	115

CHAPTER 3

FUNDAMENTALS OF ALTERNATING CURRENT

3.1	INTRODUCTION	119
3.2	GENERATION OF ALTERNATING VOLTAGES & CURRENTS	119
3.2.1	D.C. Waveform or Steady Waveform	120
3.2.2	A.C. Waveforms	120
3.2.3	Periodic and Aperiodic Waveforms	121
3.2.4	Sinusoidal Waveforms	123
3.2.5	Generation of Sinusoidal Waveforms	124
3.3	EXPRESSION FOR THE E.M.F. GENERATED BY A SINGLE PHASE ALTERNATOR	126
3.3.1	Time Period (T)	128
3.3.2	Amplitude	128
3.3.3	Cycle	128
3.3.4	Frequency	128
3.3.5	Relation between Frequency and Time Period	128
3.3.6	Relation between Frequency and Angular Velocity	129
3.3.7	Relationship Between Frequency, Speed And Number of Pole Pairs ...	129
3.3.8	Average Value Of An Alternating Current	130
3.3.9	Root Mean Square (RMS) Value Of An Alternating Current	133
3.3.10	Form Factor And Peak Factor	137
3.4	DIFFERENT FORMS OF REPRESENTING ALTERNATING QUANTITIES	140
3.4.1	Phasor Representation of an Alternating Quantity	140
3.4.2	Lagging / Leading Waveforms With Phase & Phase Difference	143
3.4.3	Rectangular Coordinates Representation	144
3.4.3.1	j-Operator	144
3.4.3.2	Phasor Represented in Rectangular Coordinate Components	145
3.4.3.3	Trigonometrical Form of Phasor Representation	146
3.4.3.4	Exponential Form of Phasor Representation	147
3.4.3.5	Polar Form of Phasor Representation	147

3.5	ARITHMETIC OPERATIONS OF PHASORS	148
3.5.1	Addition and Subtraction of Phasors	148
3.5.2	Multiplication and Division of Phasors	149
3.5.3	Power and Roots of Vectors	150
	3.5.3.1 Powers	150
	3.5.3.2 Roots	150
3.5.4	Conjugate of a Phasor and Rationalization	151
3.6	INSTANTANEOUS & AVERAGE POWER IN A.C. CIRCUITS	155
3.6.1	A.C. Circuit with Pure Resistance As Load (3.6.5a)	156
3.6.2	A.C. Circuit with Pure Inductance as Load	159
3.6.3	A.C. Circuit with Pure Capacitance as Load	162
	COMPREHENSION - 3	168
	EXERCISE - 3	170

CHAPTER 4

A.C. SINGLE PHASE AND THREE PHASE CIRCUITS

4.1	INTRODUCTION	173
4.2	POWER AND POWER FACTOR IN SINGLE PHASE A.C. CIRCUITS	174
4.3	A.C. SERIES CIRCUITS	174
4.3.1	R-L Series Circuit with A.C. Supply	174
4.3.2	Power Factor	177
4.3.3	Voltage Drop Triangle	178
4.3.4	Complex Power	178
4.3.5	VA or KVA Triangle	180
4.3.6	Wattfull and Wattless Component of Current	181
4.3.7	R-C Series Circuit with A.C. Supply	183
4.3.8	Power Factor	187
4.3.9	Voltage Drop Triangle	187
4.3.10	Complex Power	187
4.3.11.	VA or KVA Triangle	189

4.3.12	Wattfull and Wattless Component of Current	189
4.3.13.	Admittance & Admittance Triangle	191
4.3.14	R-L-C Series Circuit	193
4.3.15.	A.C. Series Circuit with Two or More Impedances	195
4.4	A.C. PARALLEL CIRCUITS	196
4.4.1	A.C. Parallel Circuit with Two or More Impedances	197
4.5	A.C. SERIES - PARALLEL CIRCUIT	199
4.6	A.C. STAR - DELTA CONNECTED CIRCUITS	203
4.7.	IMPORTANCE OF POWER FACTOR	208
4.8	FEATURES OF A.C. SINGLE PHASE CIRCUITS	208
4.9	USES OF A.C. SINGLE PHASE CIRCUITS	209
4.10	INTRODUCTION TO THREE-PHASE SYSTEMS	210
4.11	POLY-PHASE SYSTEM	210
4.12	ADVANTAGES OF THREE PHASE SYSTEMS	211
4.13	GENERATION OF THREE-PHASE E.M.F.S	211
4.13.1	Phasor Diagram	213
4.13.2	Phase Sequence	214
4.13.3	Change of Phase Sequence	215
4.14	BALANCED & UNBALANCED THREE-PHASE CIRCUITS	215
4.14.1	Balanced Three-Phase System	215
4.14.2	Unbalanced Three-Phase System	216
4.15	THREE PHASE CONNECTIONS	216
4.15.1	Six Line Conductors	217
4.15.2	Star or WYE Connection with 3 wires or 4 wires	217
4.15.3	Delta or Mesh Connection	218
4.16	THREE-PHASE VOLTAGES&CURRENTS-PHASE & LINE VALUES ..	221
4.16.1	Star Connection - Phase & Line Voltages	221
4.16.2	Star Connection - Phase & Line Currents	222
4.16.3	Delta Connection - Phase & Line Voltages	223
4.16.4	Delta Connection - Phase & Line Currents	224

4.17	BALANCED OR UNBALANCED THREE - PHASE LOADS	226
4.17.1	Three-Phase Balanced Load	226
4.17.2	Three-Phase Unbalanced Load	234
4.17.3	Line & Phase Values of Voltages & Currents - Phasor Relationships ..	237
4.17.3.1	Star Connected Load	237
4.17.3.2	Delta Connected Load	239
4.18	POWER IN THREE - PHASE CIRCUITS	246
4.19	POWER MEASUREMENT IN THREE - PHASE CIRCUITS	247
4.20.	THREE WATTMETER METHOD	249
4.21	TWO-WATTMETER METHOD	250
4.22	TWO WATTMETER METHOD FOR BALANCED LOAD	252
4.22.1	Power Measurement for Star Connected Load	253
4.22.2	Determination of Power Factor from Wattmeter Readings	255
4.22.3	Power Measurement for Delta Connected Load	255
4.22.4	Determination of Reactive Power from two Wattmeter Reading	255
4.23	EFFECT OF POWER FACTOR ON THE WATTMETER READINGS	256
4.24	LEADING POWER FACTOR	258
4.25.	OTHER METHODS OF CONNECTING TWO WATTMETERS	259
4.26	SINGLE WATTMETER METHOD	261
4.27	MEASUREMENT OF REACTIVE POWER	261
4.28	THREE PHASE WATTMETER	263
4.29	POWER FACTOR METER	263
4.30	PHASE SEQUENCE METER	270
4.31	FREQUENCY METER.....	270
4.32	COMPARISON BETWEEN STAR & DELTA CONNECTIONS	271
4.33	COMPARISON BETWEEN 1-PHASE & 3-PHASE SUPPLY SYSTEMS ..	272
	COMPREHENSION - 4.....	273
	EXERCISE - 4	277

UNIT - II

CHAPTER 5

MAGNETIC CIRCUITS & ELECTROMAGNETIC INDUCTION

5.1	INTRODUCTION.....	285
5.2	MAGNETIC CIRCUITS	285
5.2.1	Magnetization or Magnetizing Force (H)	285
5.2.1.1	Right Hand Screw Rule	286
5.2.1.2	Right Hand Thumb Rule	286
5.2.1.3	Right Hand Grip Rule	286
5.2.2	Magnetic Flux Density	287
5.2.3	Magnetic Flux	287
5.2.4	Magnetic Circuits	287
5.2.5	Permeance	288
5.2.6	Reluctivity	288
5.2.7	Leakage Flux	288
5.2.7.1	Leakage Coefficient or Leakage Factor	289
5.2.7.2	Fringing	289
5.2.7.3	Ampere-Turns Calculations	292
5.2.8	Series Magnetic Circuit	293
5.2.9	Parallel Magnetic Circuit	300
5.3	MAGNETIZATION CURVE OR B-H CURVE	304
5.3.1	Magnetic Calculations from B-H Curves	306
5.4	MAGNETIC HYSTERESIS	307
5.4.1	Residual Magnetism and Retentivity	308
5.4.2	Coercive Force	309
5.4.3	Hysteresis Loss	309
5.4.4	Magnitude of Hysteresis Loss	310
5.4.5	Importance Of Hysteresis Loop	311
5.4.6	Methods of Reducing Hysteresis Loss	313

5.5	EDDY CURRENT LOSS	314
5.5.1	Method of Reducing Eddy Current Loss	315
5.5.2	Core Loss	315
5.6	FARADAY'S LAWS OF ELECTROMAGNETIC INDUCTION	316
5.6.1	First Law	316
5.7	DIRECTION OF INDUCED E.M.F.	319
5.7.1	Fleming's Right Hand Rule	319
5.7.2	Lenz's Law	319
5.8	INDUCED E.M.F.	320
5.9	DYNAMICALLY INDUCED E.M.F.	321
5.10	STATICALLY INDUCED E.M.F.	324
5.10.1	Self Induced E.M.F.	324
5.10.2	Mutually Induced E.M.F.	326
5.10.3	Force on a Current Carrying Conductor in a Magnetic Field	327
5.10.4	Force Between Two Parallel Conductors in a Magnetic Field	328
5.11	LIFTING POWER OF MAGNET	332
	COMPREHENSION - 5	335
	EXERCISE - 5	337

CHAPTER 6

TRANSFORMERS

6.1	INTRODUCTION	341
6.2	USES OF TRANSFORMERS	342
6.3	PRINCIPLE OF OPERATION OF A TRANSFORMER	342
6.4	IDEAL TRANSFORMER	343
6.5	TRANSFORMER CONSTRUCTION	343
6.6	E.M.F EQUATION OF TRANSFORMER	345
6.7	TRANSFORMER ON NO LOAD	348
6.8	TRANSFORMER ON LOAD	349

6.9. REGULATION OF A TRANSFORMER	353
6.10. OPEN CIRCUIT AND SHORT-CIRCUIT TESTS ON TRANSFORMER ..	353
6.11 OPEN CIRCUIT OR NO LOAD TEST	353
6.11.1 Short Circuit Tests	354
6.12. EQUIVALENT CIRCUIT OF A TRANSFORMER.....	358
6.13. EFFICIENCY OF A TRANSFORMER	361
6.14. TRANSFORMER EFFICIENCY :	362
6.15. CONDITION FOR MAXIMUM EFFICIENCY :	362
6.16. ALL-DAY EFFICIENCY	366
6.17 AUTO TRANSFORMERS	367
COMPREHENSION - 6	371
EXERCISE - 6	372

UNIT - III

CHAPTER 7

D.C. MACHINES

7.1 INTRODUCTION.....	375
7.2 GENERATOR PRINCIPLE	375
7.3 PARTS OF A D.C. GENERATOR	376
7.4 PRINCIPLE OF OPERATION.....	379
7.5 E.M.F. INDUCED IN THE GENERATOR	382
7.6 NO LOAD MAGNETIZATION CURVE	384
7.7 THE VOLTAGE BUILD-UP PHENOMENON :	385
7.8 REASONS FOR A GENERATOR NOT BUILDING UP :	386
7.9 TYPES OF GENERATORS	387
7.10 LOAD CHARACTERISTICS	388
7.11 APPLICATIONS OF DC GENERATORS	395
7.12 ARMATURE REACTION	395

7.13	INTRODUCTION.....	396
7.14	PRINCIPLE OF OPERATION.....	396
7.15	BACK EMF	397
7.16	TORQUE DEVELOPED:.....	398
7.17	SPEED EQUATION:.....	402
7.18	CHARACTERISTICS OF D.C. MOTORS:.....	403
7.19	COMPOUND MOTORS	405
7.20	APPLICATIONS OF D.C. MOTORS:.....	406
7.21	STARTERS FOR D.C. MOTORS:.....	407
7.22	CHANGING THE DIRECTION OF ROTATION:.....	409
7.23	SPEED CONTROL OF D.C. MOTORS:.....	409
7.24	EFFICIENCY OF D.C. MACHINES:	420
7.25	TESTING OF D.C. MACHINES:.....	424
	COMPREHENSION - 7	430
	EXERCISE - 7	432

CHAPTER 8

A.C MACHINES - I SYNCHRONOUS MACHINES

8.1	INTRODUCTION.....	439
8.2	PRINCIPLE OF OPERATION OF AN ALTERNATOR	440
8.3	ARRANGEMENT OF WINDINGS	440
8.4	CONSTRUCTIONAL DETAILS.....	441
8.5	EMF EQUATION OF AN ALTERNATOR	441
8.6	VOLTAGE DROP IN AN ALTERNATOR	444
8.7	VOLTAGE REGULATION	445
8.8	INTRODUCTION.....	448
8.9	ROTATING MAGNETIC FIELD	448
8.10	THE SYNCHRONOUS MOTOR ON LOAD	450
8.11	SYNCHRONOUS MOTOR CHARACTERISTICS	450

8.12 APPLICATIONS OF SYNCHRONOUS MOTORS	451
COMPREHENSION - 8	452
EXERCISE - 8	453

CHAPTER 9

A.C. MACHINES - II INDUCTION MOTORS

9.1 INTRODUCTION	455
9.2 CONSTRUCTION	455
9.3 PRODUCTION OF ROTATING MAGNETIC FIELD	456
9.4 MATHEMATICAL PROOF	460
9.5 PRINCIPLE OF OPERATION	460
9.6 FREQUENCY OF ROTOR E.M.F. AND CURRENT	461
9.7 TORQUE OF AN INDUCTION MOTOR	463
9.8 TORQUE SLIP CURVE.....	464
9.9 STARTING OF THREE-PHASE INDUCTION MOTORS	465
9.10 COMPARISON OF INDUCTION MOTORS AND SYNCHRONOUS MOTORS	466
9.11 SINGLE-PHASE INDUCTION MOTORS	466
9.12 SPLIT-PHASE MOTOR.....	467
9.13 CAPACITOR START MOTORS	467
9.14 CAPACITOR START AND RUN MOTOR	468
9.15 SHADED-POLE MOTORS	468
COMPREHENSION - 9	469
EXERCISE - 9	470

UNIT - IV

CHAPTER 10

DIGITAL ELECTRONICS

10.1	INTRODUCTION	471
10.1.1	Decimal Number System	471
10.1.2	Binary Number System	472
10.1.3	Octal Number System	473
10.1.4	Hexadecimal number system	473
10.2	CONVERSION OF NUMBER SYSTEM	473
10.2.1	Decimal to binary conversion	474
10.2.2	Decimal to Octal Conversion	475
10.2.3	Decimal to hexadecimal conversion	476
10.2.4	Binary to Octal Conversion	477
10.2.5	Binary to Decimal Conversion	477
10.2.6	Binary to Hexadecimal Conversion	478
10.2.7	Octal to Binary Conversion	478
10.2.8	Octal to Decimal Conversion	479
10.2.9	Octal to Hexadecimal Conversion	479
10.2.10	Hexadecimal to Binary Conversion	480
10.2.11	Hexadecimal to Octal Conversion	480
10.2.12	Hexadecimal to Decimal Conversion	481
10.3	AIRTHMETIC OPERATION	482
10.3.1	Binary addition	482
10.3.2	Binary Subtraction	482
10.3.3	Binary Multiplication	483
10.3.4	Binary Division	483
10.4	COMPLEMENTS	484
10.4.1	r's Complements	484
10.4.2	(r – 1)'s Complement	485

10.4.3	Advantage and Disadvantage of 1's and 2's complement	487
10.4.4	Subtraction with 1's Complement	488
10.4.5	Subtraction with 2's Complement	488
10.5	SIGNED NUMBERS	489
10.5.1	Sign Magnitude Representation	489
10.5.2	1's Complement Representation	490
10.5.3	2's Complement Representation	491
10.6	FLOATING POINT	491
10.7	DE-MORGAN'S THEOREM.....	492
10.7.1	Law 1	492
10.7.2	Law 2	493
10.8	LOGIC GATES.....	494
10.8.1	Basic Gates	494
10.8.2	Universal Gates	497
10.8.3	Universality or Realization of NAND and NOR Gates	498
10.8.4	Special Gates	500
10.9	ADDERS	501
10.9.1	Half Adder	501
10.9.2	Full Adder	502
10.10	FLIP-FLOP	504
10.10.1	NAND Gate Latch	505
10.10.2	NOR Gate Latch	506
10.10.3	Clocked Flip-Flops	506
10.10.4	R-S Flip-Flop	506
10.10.5	J-K Flip Flop	508
10.11	SOLVED QUESTIONS	509
10.12	QUESTIONS	511

UNIT - V

CHAPTER 11

ELECTRONIC COMPONENTS AND CIRCUITS

11.1	SEMICONDUCTOR.....	513
11.1.1	Introduction	514
11.1.2	Intrinsic Semiconductor	514
11.1.3	Intrinsic Concentration of a Semiconductor is given by the Relation	515
11.1.4	Resistivity of Intrinsic Semiconductor Material	515
11.1.5	Current in Intrinsic Semiconductor	515
11.1.6	Conductivity of Intrinsic Semiconductor Material	515
11.1.7	Current Density (J)	516
11.1.8	Extrinsic Semiconductor	516
11.1.9	N-type Extrinsic Semiconductor	516
11.1.10	P-type Extrinsic Semiconductor	517
11.2	DIODES	518
11.2.1	Biasing of a Diode	519
11.2.2	Forward Biasing	520
11.2.3	Reverse Biasing	521
11.2.4	V-I Characteristics of Diode	522
11.2.5	Threshold Voltage or I	523
11.2.6	Breakdown Voltage (V_{BR})	523
11.3	TYPES OF DIODES	523
11.3.1	Zener diode	523
11.3.2	Tunnel Diode	525
11.3.3	Varactor Diode	527
11.3.4	PIN Diode	528

11.3.5	Schottky Diode	528
11.3.6	LED (Light Emitting Diode)	529
11.3.7	Photo Diode	530
11.4	BJT (BIPOLAR JUNCTION TRANSISTOR)	531
11.4.1	Introduction	531
11.4.2	Construction	531
11.4.3	Structure and Symbol of both type of Transistor	532
11.4.4	Transistor Biasing	532
11.4.5	Transistor Current	533
11.4.6	Modes of Operation of a Transistor	533
11.4.7	Working of Transistor	533
11.4.8	Configuration of Transistor	534
11.4.9	Common base Configuration (CB)	534
11.4.10	Current Amplification Factor for CB configuration	535
11.4.11	Common Emitter Configuration	535
11.4.12	Current gain or Current Amplification Factor	536
11.4.13	Relation between α and β	536
11.4.14	Common Collector Configuration (CC)	537
11.4.15	Current Amplification Factor or Current gain	537
11.4.16	DC Biasing of a Transistor	539
11.4.17	Operating Point or Quiescent Point	539
11.4.18	DC load line	540
11.4.19	Types of Biasing Circuits	541
11.4.20	Fixed bias Circuit	541
11.4.21	Collector to base bias circuit	542
11.4.22	Self bias or emitter bias circuit	543
11.5	QUESTIONS	544

CHAPTER 12

CATHODE RAY OSCILLOSCOPE

12.1	INTRODUCTION OF CRO	547
12.2	BLOCK DIAGRAM OF CRO	547
12.3	THE DESCRIPTION OF EACH PART OF CRO IS GIVEN AS	548
12.3.1	Power supply	548
12.3.2	Vertical amplifiers	548
12.3.3	Trigger circuit	549
12.3.4	Time base generator	549
12.3.5	Horizontal Amplifier	549
12.3.6	Cathode ray tube	549
12.3.7	Delay line	549
12.4	PRINCIPLES OF CATHODE RAY OSCILLOSCOPE	549
12.4.1	Electron gun assembly	550
12.4.1.1	Cathode	550
12.4.1.2	Control grid	550
12.4.1.3	Accelerating electrode	550
12.4.1.4	Focusing anode	550
12.4.1.5	Accelerating anode	551
12.4.2	Deflection plate	551
12.4.3	Fluorescent screen	551
12.4.4	Glass body and base	551
12.5	FOCUSING	552
12.5.1	Electrostatic focusing	552
12.5.2	Electromagnetic focusing	552

12.6	DEFLECTION AND SENSITIVITY	552
12.6.1	Electrostatic deflection and deflection sensitivity	552
	12.6.1.1 Deflection sensitivity	555
12.6.2	Electromagnetic deflection and deflection sensitivity	555
	12.6.2.2 Deflection Sensitivity	557
12.7	VARIOUS CONTROL PANNELS OF CRO	557
12.7.1	Intensity Control	557
12.7.2	Focus Control	557
12.7.3	Shift Control	557
12.7.4	Synchronization Control	558
12.7.5	Gain Control	558
12.8	APPLICATION OF CRO	558
12.8.1	Voltage measurement	558
12.8.2	Current measurement	559
12.8.3	Frequency measurement	559
	QUESTIONS	560
	REFERENCES	561