

---

## CONTENTS

---

<i>Preface</i> .....	(vii)
<i>Symbols</i> .....	(xlx)
<i>Brief History of Electronics</i> .....	(xxiii)

### **Chapter 1**

<b>Semiconductor and Magnetic Material</b>	<b>1-11</b>
1.1    Introduction .....	2
1.2    Semiconductor Materials (Group-IV) .....	2
1.3    Opto-Electronic Devices Semiconductor Materials .....	4
1.4    Energy Bands and Electrical Conduction .....	8
1.5    Semi-insulators .....	9
1.6    Magnetic Semiconductors .....	9
<i>Summary</i> .....	9
<i>Multiple Choice Questions</i> .....	10
<i>Long Questions</i> .....	49

### **Chapter 2**

<b>Electron Dynamics and CRO</b>	<b>11-50</b>
2.1    Electron Dynamics .....	12
2.2    Motion of Charged Particles in Electric and Magnetic Fields .....	12
2.3    Simple Problems Involving Electric and Magnetic Fields Only .....	34
2.4    Principles of CRT .....	36
2.5    Deflection Sensitivity .....	39
2.6    Applications of CRO .....	46

---

<i>Summary</i> .....	46
<i>Objective Type Questions</i> .....	47
<i>Essay Type Questions</i> .....	48
<i>Multiple Choice Questions</i> .....	48
<i>Conceptual Questions</i> .....	49

**Chapter 3**

<b>Junction Diode Characteristics</b>	<b>51-148</b>
3.1    Review of Semiconductor Physics .....	52
3.2    Energy Band Structures .....	73
3.3    Conduction in Semiconductors .....	74
3.4    Conductivity of an Intrinsic Semiconductor .....	78
3.5    Donor Type or n-Type Semiconductors .....	79
3.6    Acceptor Type or p-Type Semiconductors .....	80
3.7    Ionization Energy .....	80
3.8    Holes and Electrons .....	80
3.9    Mass Action Law .....	82
3.10    Law of Electrical Neutrality.....	82
3.11    The Fermi Dirac Function .....	87
3.12    Total Current in a Semiconductor .....	96
3.13    Einstein Relationship .....	102
3.14    Continuity Equation.....	102
3.15    The Hall Effect .....	104
3.16    Semiconductor Diode Characteristics .....	108
3.17    The p-n Junction Diode in Reverse Bias .....	110
3.18    The p-n Junction Diode in Forward Bias .....	110
3.19    Band Structure of an Open Circuit p-n Junction .....	111
3.20    The Current Components in a p-n Junction Diode .....	114
3.21    Law of the Junction .....	115
3.22    Diode Current equation .....	116
3.23    Volt-Ampere Characteristics of a p-n Junction diode .....	117
3.24    Temperature Dependence of p-n Junction Diode Characteristics .....	119

---

3.25	Space Charge or Transition Capacitance $C_T$ .....	120
3.26	Diffusion Capacitance, $C_D$ .....	123
3.27	Diode Switching Times .....	125
3.28	Break Down Mechanism .....	130
3.29	Zener Diode .....	131
3.30	The Tunnel Diode .....	132
3.31	Varactor Diode .....	135
	<i>Summary</i> .....	141
	<i>Objective Type Questions</i> .....	142
	<i>Essay Type Questions</i> .....	143
	<i>Multiple Choice Questions</i> .....	144
	<i>Conceptual Questions</i> .....	146

**Chapter 4**

	<b>Rectifiers, Filters and Regulators</b>	<b>150-198</b>
4.1	Rectifiers .....	150
4.2	Half-Wave Rectifier .....	150
4.3	Full Wave Rectifier ( FWR ) .....	160
4.4	Bridge Rectifiers .....	164
4.5	Comparison of Rectifier Circuits .....	165
4.6	Voltage Doubler Circuit .....	166
4.7	Inductor Filter Circuits .....	166
4.8	Capacitor Filter .....	171
4.9	LC Filter (L-Section Filter) .....	175
4.10	CLC or $\pi$ Filter .....	179
4.11	Multiple LC Filters .....	183
4.12	Introduction to Regulators (Zener and shunt regulators) .....	187
4.13	Terminology .....	196
	<i>Summary</i> .....	197
	<i>Objective Type Questions</i> .....	197
	<i>Essay Type Questions</i> .....	198
	<i>Multiple Choice Questions</i> .....	198

**Chapter 5**

<b>Transistor Characteristics</b>	<b>199-280</b>
5.1 Bipolar Junction Transistors ( BJT's ) .....	200
5.2 Transistor Construction .....	204
5.3 The Ebers-Moll Equation .....	205
5.4 Types of Transistor Configurations .....	206
5.5 Convention for Transistors and Diodes .....	216
5.6 Field Effect Transistor (FET) .....	227
5.7 FET Structure .....	229
5.8 FET Operation .....	233
5.9 JFET Volt-Ampere Characteristics .....	236
5.10 Transfer Characteristics of FET .....	238
5.11 FET Small Signal Model .....	242
5.12 FET Tree .....	247
5.13 The Depletion MOSFET .....	254
5.14 CMOS Structure (Complementary MOS).....	257
5.15 Silicon Controlled Rectifier .....	260
5.16 Unijunction Transistor (UJT).....	265
5.17 LED's .....	269
5.18 Photo Diodes .....	269
5.19 Photo Transistors .....	270
<i>Summary</i> .....	271
<i>Objective Type Questions</i> .....	272
<i>Essay Type Questions</i> .....	273
<i>Multiple Choice Questions</i> .....	274

**Chapter 6**

<b>Transistor Biasing and Stabilization</b>	<b>281-326</b>
6.1 Transistor Biasing .....	282
6.2 Fixed Bias Circuit or (Base Bias Circuit ) .....	284
6.3 Bias Stability .....	285

---

6.4	Thermal Instability .....	285
6.5	Stability Factor 'S' for Fixed Bias Circuit .....	286
6.6	Collector to Base Bias Circuit .....	287
6.7	Self Bias or Emitter Bias Circuit .....	290
6.8	Stability Factor 'S' for Self Bias Circuit.....	291
6.9	Stability Factor S '	292
6.10	Stability Factor S " for Self Bias Circuit .....	294
6.11	Practical Considerations.....	294
6.12	Bias Compensation Techniques .....	295
6.13	Biassing Circuits For Linear Integrated Circuits.....	298
6.14	Thermistor and Sensistor Compensation .....	299
6.15	Thermal Runaway .....	300
6.16	Stability Factor S " for Self Bias Circuit .....	306
6.17	FET Biasing.....	312
6.18	Basic FBT Circuits.....	316
	<i>Summary.....</i>	323
	<i>Objective Type Questions.....</i>	324
	<i>Essay Type Questions .....</i>	324
	<i>Multiple Choice Questions .....</i>	325
	<i>Conceptual Questions .....</i>	326

**Chapter 7**

<b>Amplifiers</b>	<b>327-394</b>	
7.1	Introduction .....	328
7.2	Black Box Theory .....	328
7.3	Transistor Hybrid Model.....	332
7.4	Transistor in Common Emitter Configuration.....	332
7.5	Determination of h-Parameters From the Characteristics of a Transistor .....	333
7.6	Common Collector Configuration ( CC ) .....	335
7.7	Hybrid Parameter Variations .....	336

---

7.8	Conversion of Parameters From C.B. to C.E. ....	337
7.9	Measurement of h-Parameters.....	339
7.10	General Amplifier Characteristics .....	341
7.11	Analysis of Transistor Amplifier Circuit Using h-Parameters .....	344
7.12	Comparison of the CE, CB, CC Configurations in terms of $A_v$ , $A_{\text{v}}$ , $R_i$ , $R_o$ .....	348
7.13	Small Signal Analysis of Junction Transistor .....	351
7.14	High Input Resistance Transistor Circuits .....	368
7.15	Boot Strapped Darlington Circuit .....	372
7.16	The Cascode Transistor Configuration .....	375
7.17	The JFET Low frequency Equivalent Circuits.....	379
7.18	Comparison of FET and BJT Characteristics .....	383
7.19	R. C. Coupled Amplifier .....	384
7.20	Concept of $f_a$ , $f_b$ and $f_T$ .....	387
	<i>Summary</i> .....	389
	<i>Objective Type Questions</i> .....	390
	<i>Essay Type Questions</i> .....	391
	<i>Multiple Choice Questions</i> .....	392
	<i>Conceptual Questions</i> .....	394

**Chapter 8**

<b>Frequency Response</b>	<b>395-455</b>	
8.1	Introduction .....	396
8.2	Definiciton of Cut-off Frequency and Bandwidth .....	397
8.3	Effect of Various Capacitors on Frequency Response .....	419
8.4	Low-Frequency Response of Common-Emitter Amplifier .....	420
8.5	Low-Frequency Response of Common Source Amplifier.....	425
8.6	High-Frequency Response of Common-Emitter Amplifier .....	428
8.7	High-Frequency Response of Common-Source Amplifier .....	433
8.8	Two-Stage RC-Coupled CE-CE Cascade Amplifier .....	438
8.9	Two-State RC-Coupled CE-CB Cascade Amplifier .....	439
8.10	Two-Stage RC-Coupled CE-CC Amplifier .....	446

---

8.11	Low-Frequency Response of Source Follower .....	450
	<i>Summary</i> .....	452
	<i>Self Test</i> .....	452
	<i>Long Questions</i> .....	454

**Chapter 9**

<b>Feedback Amplifiers</b>	<b>456-503</b>	
9.1	Feedback Amplifiers .....	457
9.2	Classification of Amplifiers .....	457
9.3	Feedback Concept .....	460
9.4	Types of Feedback .....	462
9.5	Effect of Negative Feedback on Transfer Gain .....	462
9.6	Transfer Gain with Feedback .....	467
9.7	Classification of Feedback Amplifiers .....	471
9.8	Effect of Feedback on Input Resistance .....	472
9.9	Effect of Negative Feedback on $R_o$ .....	475
9.10	Analysis of Feedback Amplifiers .....	481
	<i>Summary</i> .....	499
	<i>Objective Type Questions</i> .....	500
	<i>Essay Type Questions</i> .....	501
	<i>Multiple Choice Questions</i> .....	502
	<i>Conceptual Questions</i> .....	503

**Chapter 10**

<b>Multistage Amplifier and Tuned Amplifier</b>	<b>504-549</b>	
10.1	Introduction .....	505
10.2	Cascade Amplifier .....	505
10.3	Amplifier Coupling .....	508
10.4	Different Coupling Used in Multistage Amplifier .....	508
10.5	Effect of Coupling Capacitor on Low Frequency Response .....	525
10.6	Emitter Follower .....	526
10.7	Source Follower .....	527

---

10.8	Darlington Connection .....	527
10.9	Boot Strapping .....	532
10.10	Tuned Amplifier .....	534
	<i>Solved Examples</i> .....	544
	<i>Summary</i> .....	546
	<i>Objective Type Questions</i> .....	547
	<i>Essay Type Questions</i> .....	547
	<i>Multiple Choice Questions</i> .....	548
	<i>Self-Test</i> .....	547

**Chapter 11**

<b>Large Signal (Power) Amplifiers</b>	<b>550-586</b>	
11.1	Voltage Amplifier and Power Amplifier: A Difference .....	552
11.2	Transistor Power Amplifier: Single Ended .....	554
11.3	Direct Coupled Class-A Amplifier with Resistive Load .....	558
11.4	Transformer Coupled Class-A Amplifier .....	561
11.5	Class-A Push-Pull Amplifier .....	565
11.6	Class-B Amplifier .....	568
11.7	Class-C Amplifier .....	570
11.8	Class-B Push-Pull Amplifier .....	571
11.9	Complementary Symmetry Push-Pull Class-B Amplifier .....	575
11.10	Class-AB Operation and Cross-Over Distortion .....	576
11.11	Thermal Runaway .....	578
11.12	Power Consideration and Heat-Sinks .....	579
	<i>Summary</i> .....	580
	<i>Essay Type Questions</i> .....	585
	<i>Problems</i> .....	586

**Chapter 12**

<b>Oscillators</b>	<b>587-612</b>	
12.1	Oscillators .....	588
12.2	Sinusoidal Oscillators .....	591

---

12.3	Barkhausen Criterion .....	591
12.4	R – C Phase-Shift Oscillator (Using JFET) .....	592
12.5	Transistor RC Phase-Shift Oscillator .....	595
12.6	A General form of LC Oscillator Circuit .....	598
12.7	Loop Gain .....	598
12.8	Wien Bridge Oscillator .....	601
12.9	Expression for $f$ .....	602
12.10	Thermistor .....	603
12.11	Sensistor .....	603
12.12	Amplitude Stabilization .....	603
12.13	Applications .....	604
12.14	Resonant Circuit Oscillators .....	604
12.15	Crystal Oscillators .....	605
12.16	Frequency Stability .....	606
12.17	Frequency of Oscillations for Parallel Resonance Circuit .....	607
12.18	1-MHz FET Crystal Oscillator Circuit .....	607
	<i>Summary</i> .....	608
	<i>Objective Type Questions</i> .....	609
	<i>Essay Type Questions</i> .....	610
	<i>Multiple Choice Questions</i> .....	611
	<i>Conceptual Questions</i> .....	612

**Chapter 13**

	<b>Operational Amplifier</b>	<b>607-661</b>
13.1	Introduction .....	616
13.2	Ideal Op-Amp .....	616
13.3	Op-loop Op-amp Configuration .....	623
13.4	Block Diagram of Op-amp .....	625
13.5	The Switch Hitter .....	640
13.6	The Instrumentation Amplifier .....	641
13.7	Low Pass Amplifiers: The Inverting Low-Pass Amplifiers .....	643
13.8	High Pass Amplifiers .....	646
13.9	The Op-amp as a Comparator .....	649

---

13.10	Advantages of Negative Feedback .....	652
13.11	Logarithmic Amplifier using Op-amp .....	653
13.12	Antilogarithmic Amplifier .....	655
	<i>Summary</i> .....	655
	<i>Short Problem</i> .....	656
	<i>Essay Type Problems</i> .....	656
	<i>Multiple Type Questions</i> .....	658

**Chapter 14****Multivibrators 663-694**

14.1	Introduction .....	664
14.2	Multivibrators and their Principle .....	664
14.3	Multivibrators using BJTS .....	665
14.4	Voltage Multipliers .....	669
14.5	Precision Rectifier .....	670
14.6	Sample and Hold Circuit .....	674
14.7	Op-amp Square Wave Generator (Astable Multivibrator) .....	676
14.8	Triangular Wave Generator .....	680
14.9	Saw Tooth Wave Generator (Ramp generator) .....	681
14.10	555-Time IC .....	683
14.11	Bistable Multivibrator using Op-amp .....	690
	<i>Summary</i> .....	691
	<i>Objective Type Questions</i> .....	692
	<i>Long Problems</i> .....	694

**Appendix .....** 695-728**Answers .....** 729-739**Index .....** 741-743