

Contents

<i>Preface</i>	(vii)
----------------------	-------

CHAPTER 1

Introduction to Electrical Energy and DC Circuits

1.1 Introduction.....	1
1.1.1 The Role of Electrical Energy in Modern Life.....	1
1.1.2 Electrical Energy vs Computer Science Engineering.....	2
1.2 Over View of Electrical Energy Generation, Transmission and Utilization.....	2
1.3 Electric Circuit.....	4
1.3.1 Circuit Elements.....	5
1.3.2 Electrical Energy Sources	8
1.4 Source Transformation	13
1.5 Kirchhoff's Laws	16
1.6 Problems on Series-Parallel Connections	31
1.7 Star/Delta Transformations.....	36
1.8 Superposition Theorem.....	48
1.9 Thevenin's Theorem	51
1.10 Time Response of RL and RC Circuits	62
1.10.1 Introduction to Transients	62
1.10.2 DC Response of an R-L Circuit	62
1.10.3 DC Response of an R-C Circuit	66
<i>Review Questions</i>	70
<i>Short Answer (Two marks) Questions</i>	70
<i>Essay (Six marks) Questions</i>	71

CHAPTER 2

Steady State A.C Circuits

2.1.1 Representation of Sinusoidal Waveforms	73
2.1.2 Average and RMS Values	80
2.2 Analysis of Single Phase AC Circuits	89
2.2.1 A.C through Pure Resistance.....	89
2.2.2 AC through Pure Inductance	90
2.2.3 A.C through Pure Capacitance	93
2.2.4 AC through Series R-L Circuit.....	96
2.2.5 AC through Series R-C Circuit	98
2.2.6 AC through Series R-L-C Circuit.....	100
2.3 Three Phase Balanced Circuits	112
2.3.1 Star Connection	114
2.3.2 Delta Connection.....	117
<i>Review Questions</i>	129
<i>Short Answer (Two marks) Questions</i>	129
<i>Essay (Six marks) Questions</i>	129

CHAPTER 3

Transformers and DC Machines

3.1 Transformers.....	130
3.1.1 Working Principle	130
3.1.2 Brief Construction of Transformers	132
3.1.3 Emf Equation.....	132
3.1.4 Transformer on No-load.....	137
3.1.5 Ideal Transformer	139
3.1.6 Real Transformer or Practical Transformer	139
3.1.7 Transformer Equivalent Circuit.....	141
3.1.8 Voltage Regulation.....	144
3.1.9 Losses and Efficiency.....	149
3.2 DC Machines	158
3.2.0 Introduction	158
3.2.1 DC Generators.....	158
3.2.2 DC Generator Principle.....	159

3.2.3	Simple Loop Generator	161
3.2.4	Construction	163
3.2.5	Emf Generated or EMF equation	166
3.2.6	Classification of DC Generators.....	169
3.3	DC Motors	171
3.3.1	DC Motor Principle	172
3.3.2	Back Emf.....	173
3.3.3	Classification of DC Motors.....	175
3.3.4	Load Characteristics of a Separately Excited DC Motor	178
3.3.5	Speed Control of Separately Excited DC Motor	181
	<i>Review Questions</i>	184
	<i>Short Answer (Two marks) Questions</i>	184
	<i>Essay (Six marks) Questions</i>	185

CHAPTER 4

Alternating Current Machines

4.1	Three Phase Induction Motors	186
4.1.1	Introduction	186
4.1.2	Construction	186
4.1.3	Principle	188
4.1.4	Torque – Slip Characteristics	195
4.2	Synchronous Generators	197
4.2.1	Principle	197
4.3	Stepper Motor	199
4.4	Electrical Installations and Batteries.....	200
4.4.1	Basic lay-out of wiring in Domestic Installations	200
4.4.2	Types of Wiring Systems	201
4.4.3	Fuse	204
4.4.4	Switch Fuse Unit (SFU)	206
4.4.5	MCB.....	206
4.4.6	MCCB	207
4.4.7	Earthing	208

4.5 Classification of Batteries.....	211
4.5.1 Lead-Acid battery.....	211
4.6 Elementary Calculations of Energy Consumption.....	214
4.7 Electrical Safety Precautions	216
<i>Review Questions</i>	217
<i>Short Answer (Two marks) Questions</i>	217
<i>Essay (Six marks) Questions</i>	217

CHAPTER 5

Semi-Conductor Devices

5.1 Introduction.....	219
5.1.1 P-N Junction Diode	220
5.1.2 V-I Characteristics of PN Junction Diode	223
5.1.3 Diode Applications.....	225
5.2 Bipolar Junction Transistor.....	230
5.2.1 Construction	230
5.2.2 Biasing of Transistors.....	231
5.2.3 Types of Transistor Configurations.....	234
5.2.4 Working of a Transistor	236
5.2.5 Transistor as an Amplifier.....	236
5.3 Power Converters.....	239
5.3.1 AC to DC Converters	240
5.3.2 DC to DC Converters	241
5.3.3 DC to AC Converters	242
5.4 Uninterruptible Power Supply (UPS)	243
<i>Review Questions</i>	244
<i>Short Answer (Two marks) Questions</i>	244
<i>Essay (Six marks) Questions</i>	244

CHAPTER 6

Op-Amps, Transducers and Data Acquisition

6.1 Operational Amplifier.....	245
6.1.2 Ideal Operational Amplifier	246
6.1.3 Commercial IC 741 Op-Amp	246

6.2 Remote Control and Monitoring.....	248
6.2.1 Transducer used to Sense Strain.....	248
6.2.2 Transducer used to sense the Temperature.....	249
6.2.3 Transducer to Sense the Acceleration	250
6.2.4 Transducer to Sense the Light	251
6.3 A/D and D/A Converters	252
6.3.1 Digital to Analog Converter (D/A Converter).....	253
6.3.2 Analog to Digital Converter	254
6.4 Data Acquisition and Control	255
<i>Review Questions</i>	256
<i>Short Answer (Two marks) Questions</i>	256
<i>Essay (Six marks) Questions</i>	257
<i>Index</i>	259